

Ohm's Law

Topics Covered in Chapter 3

3-1: The Current $I = V/R$

3-2: The Voltage $V = IR$

3-3: The Resistance $R = V/I$

3-4: Practical Units

3-5: Multiple and Submultiple Units

Topics Covered in Chapter 3

- 3-6: The Linear Proportion between V and I
- 3-7: Electric Power
- 3-8: Power Dissipation in Resistance
- 3-9: Power Formulas
- 3-10: Choosing a Resistor for a Circuit
- 3-11: Electric Shock
- 3-12: Open-Circuit and Short-Circuit Troubles

3-1—3-3: Ohm's Law Formulas

- There are three forms of Ohm's Law:
 - $I = V/R$
 - $V = IR$
 - $R = V/I$
- where:
 - I = Current
 - V = Voltage
 - R = Resistance

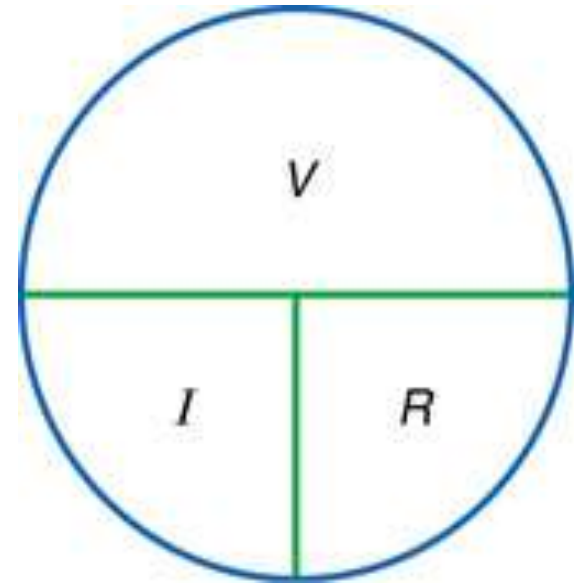


Fig. 3-4: A circle diagram to help in memorizing the Ohm's Law formulas $V = IR$, $I = V/R$, and $R = V/I$. The V is always at the top.

3-1: The Current $I = V/R$

- $I = V/R$
- In practical units, this law may be stated as:
 - amperes = volts / ohms

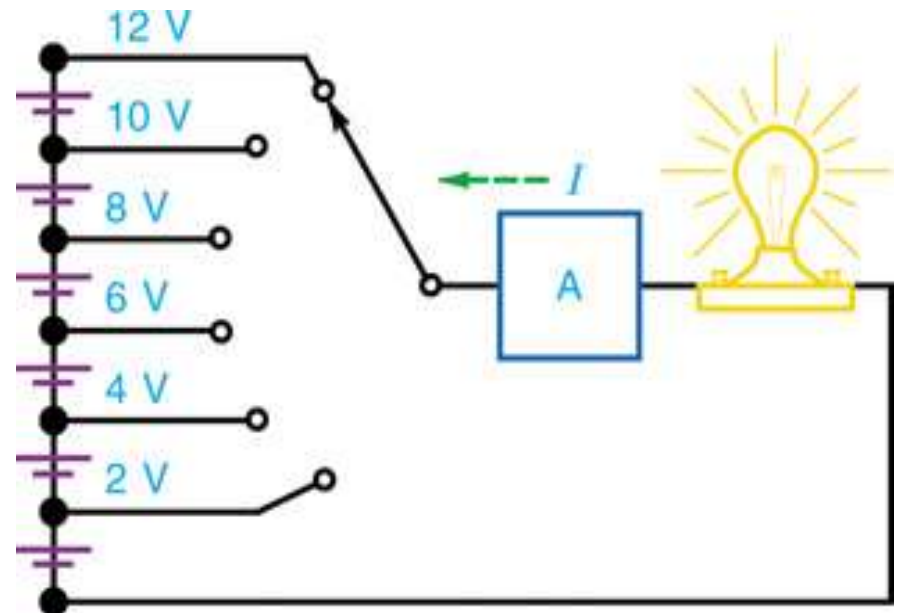






Fig. 3-1: Increasing the applied voltage V produces more current I to light the bulb with more intensity.

3-4: Practical Units

- The three forms of Ohm's law can be used to define the practical units of current, voltage, and resistance:
 - 1 ampere = 1 volt / 1 ohm
 - 1 volt = 1 ampere × 1 ohm
 - 1 ohm = 1 volt / 1 ampere

3-4: Practical Units

Applying Ohm's Law

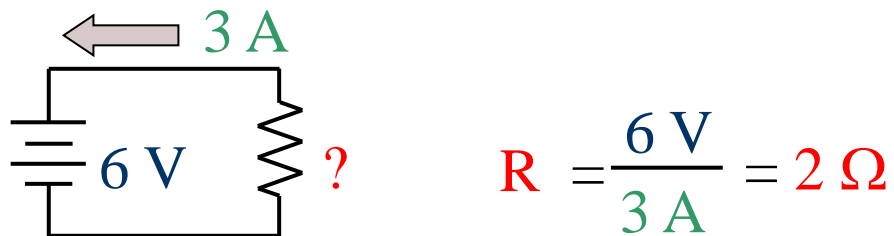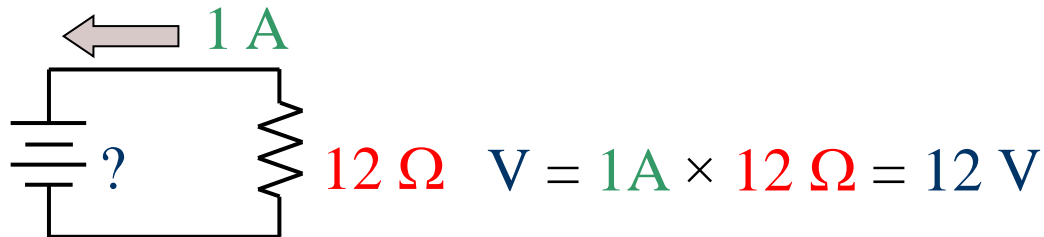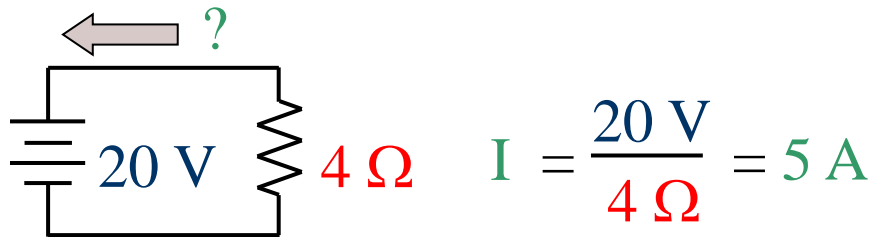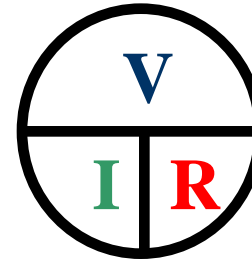

3-5: Multiple and Submultiple Units

■ Units of Voltage

- The basic unit of voltage is the **volt (V)**.

- Multiple units of voltage are:

- **kilovolt (kV)**

- 1 thousand volts or 10^3 V

- **megavolt (MV)**

- 1 million volts or 10^6 V

- Submultiple units of voltage are:

- **millivolt (mV)**

- 1-thousandth of a volt or 10^{-3} V

- **microvolt (μ V)**

- 1-millionth of a volt or 10^{-6} V

3-5: Multiple and Submultiple Units

■ Units of Current

- The basic unit of current is the **ampere (A)**.
- Submultiple units of current are:
 - **milliampere (mA)**
1-thousandth of an ampere or 10^{-3} A
 - **microampere (μ A)**
1-millionth of an ampere or 10^{-6} A


3-5: Multiple and Submultiple Units

- Units of Resistance

- The basic unit of resistance is the **Ohm (Ω)**.
- Multiple units of resistance are:
 - **kilohm (kW)**
1 thousand ohms or $10^3 \Omega$
 - **Megohm (MW)**
1 million ohms or $10^6 \Omega$

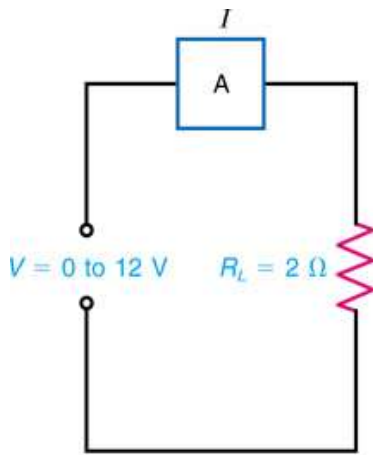3-6: The Linear Proportion between V and I


- The Ohm's Law formula $I = V/R$ states that V and I are directly proportional for any one value of R .



(a)

Volts V	Ohms Ω	Amperes A
0	2	0
2	2	1
4	2	2
6	2	3
8	2	4
10	2	5
12	2	6

(b)

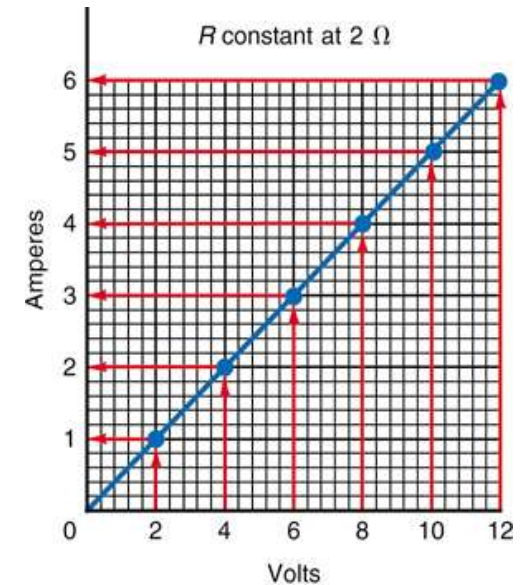

(c)

Fig. 3.5: Experiment to show that I increases in direct proportion to V with the same R . (a) Circuit with variable V but constant R . (b) Table of increasing I for higher V . (c) Graph of V and I values. This is a linear volt-ampere characteristic. It shows a direct proportion between V and I .

3-6: The Linear Proportion between V and I



- When V is constant:
 - I decreases as R increases.
 - I increases as R decreases.
- Examples:
 - If R doubles, I is reduced by half.
 - If R is reduced to $\frac{1}{4}$, I increases by 4.
 - This is known as an *inverse relationship*.

3-6: The Linear Proportion between V and I

- Linear Resistance

- A linear resistance has a constant value of ohms. Its R does not change with the applied voltage, so V and I are directly proportional.
- Carbon-film and metal-film resistors are examples of linear resistors.

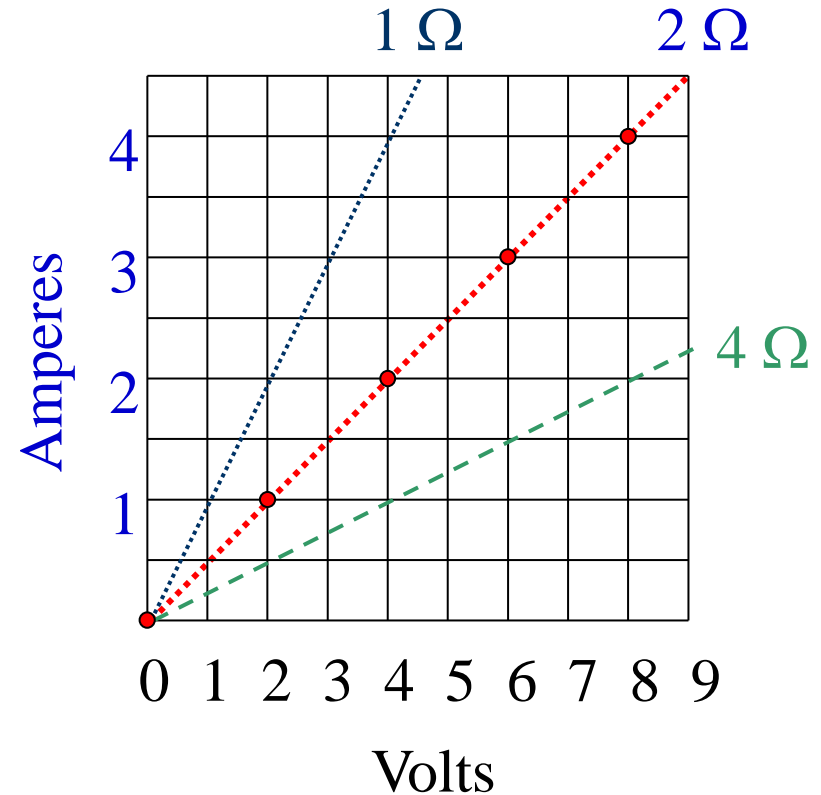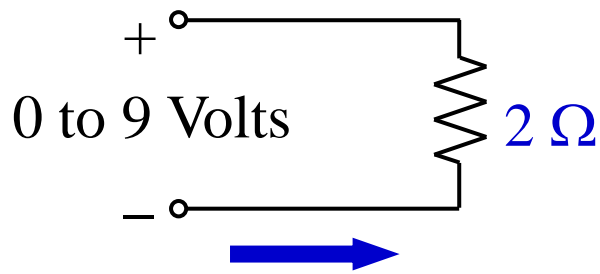3-6: The Linear Proportion between V and I





The smaller the resistor, the steeper the slope.

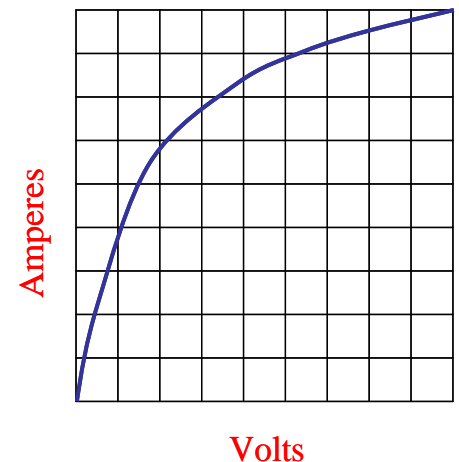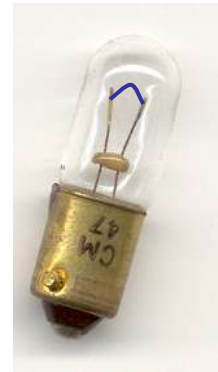3-6: The Linear Proportion between V and I



■ Nonlinear Resistance

- In a nonlinear resistance, increasing the applied V produces more current, but I does not increase in the same proportion as the increase in V .
- Example of a Nonlinear Volt–Ampere Relationship:
 - As the tungsten filament in a light bulb gets hot, its resistance increases.



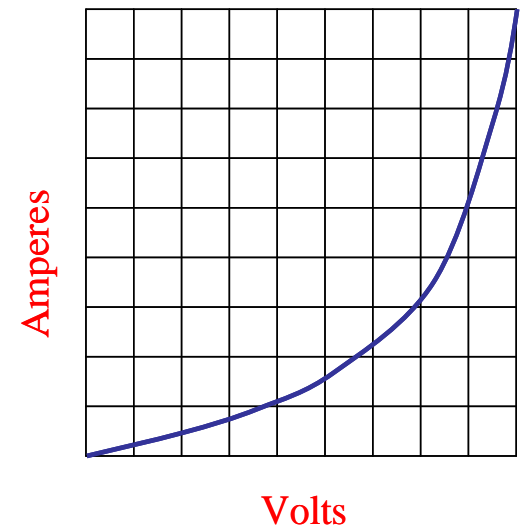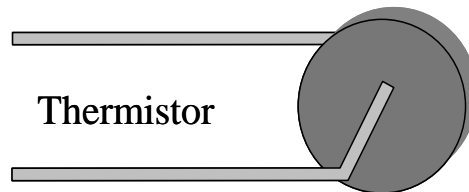3-6: The Linear Proportion between V and I

- Another nonlinear resistance is a **thermistor**.
- A thermistor is a resistor whose resistance value changes with its operating temperature.
- As an **NTC (negative temperature coefficient)** thermistor gets hot, its resistance decreases.



3-7: Electric Power

- The basic unit of power is the watt (W).
 - Multiple units of power are:
 - **kilowatt (kW):**
1000 watts or 10^3 W
 - **megawatt (MW):**
1 million watts or 10^6 W
 - Submultiple units of power are:
 - **milliwatt (mW):**
1-thousandth of a watt or 10^{-3} W
 - **microwatt (μ W):**
1-millionth of a watt or 10^{-6} W

3-7: Electric Power

- Work and energy are basically the same, with identical units.
- Power is different. It is the time rate of doing work.
 - $\text{Power} = \text{work} / \text{time}$.
 - $\text{Work} = \text{power} \times \text{time}$.

3-7: Electric Power

- Practical Units of Power and Work:
 - The rate at which work is done (power) equals the product of voltage and current. This is derived as follows:
 - First, recall that:

$$1 \text{ volt} = \frac{1 \text{ joule}}{1 \text{ coulomb}} \quad \text{and} \quad 1 \text{ ampere} = \frac{1 \text{ coulomb}}{1 \text{ second}}$$

3-7: Electric Power

Power = Volts \times Amps, or

$$P = V \times I$$

$$\text{Power (1 watt)} = \frac{1 \text{ joule}}{1 \cancel{\text{ coulomb}}} \times \frac{1 \cancel{\text{ coulomb}}}{1 \text{ second}} = \frac{1 \text{ joule}}{1 \text{ second}}$$

3-7: Electric Power

- Kilowatt Hours


- The kilowatt hour (kWh) is a unit commonly used for large amounts of electrical work or energy.
- For example, electric bills are calculated in kilowatt hours. The kilowatt hour is the billing unit.
- The amount of work (energy) can be found by multiplying power (in kilowatts) \times time in hours.

3-7: Electric Power

To calculate electric cost, start with the power:

- An air conditioner operates at 240 volts and 20 amperes.
- The power is $P = V \times I = 240 \times 20 = 4800$ watts.
 - Convert to kilowatts:
 $4800 \text{ watts} = 4.8 \text{ kilowatts}$
 - Multiply by hours: (Assume it runs half the day)
 $\text{energy} = 4.8 \text{ kW} \times 12 \text{ hours} = 57.6 \text{ kWh}$
 - Multiply by rate: (Assume a rate of \$0.08/ kWh)
 $\text{cost} = 57.6 \times \$0.08 = \$4.61 \text{ per day}$

3-8: Power Dissipation in Resistance

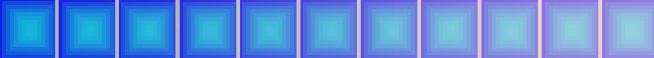- 
- When current flows in a resistance, heat is produced from the friction between the moving free electrons and the atoms obstructing their path.
 - Heat is evidence that power is used in producing current.

3-8: Power Dissipation in Resistance

- The amount of power dissipated in a resistance may be calculated using any one of three formulas, depending on which factors are known:
 - $P = I^2 \times R$
 - $P = V^2 / R$
 - $P = V \times I$

3-9: Power Formulas

There are three basic power formulas, but each can be in three forms for nine combinations.

$$P = VI$$

$$I = \frac{P}{V}$$

$$V = \frac{P}{I}$$

$$P = I^2R$$

$$R = \frac{P}{I^2}$$

$$I = \sqrt{\frac{P}{R}}$$

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P}$$

$$V = \sqrt{PR}$$

Where:

P = Power

V = Voltage

I = Current

R = Resistance

3-9: Power Formulas

- Combining Ohm's Law and the Power Formula
 - All nine power formulas are based on Ohm's Law.

$$\mathbf{V = IR}$$

$$\mathbf{I = \frac{V}{R}}$$

$$\mathbf{P = VI}$$


- Substitute IR for V to obtain:
 - $P = VI$
 - $= (IR)I$
 - $= I^2R$

3-9: Power Formulas

- Combining Ohm's Law and the Power Formula
 - Substitute V/R for I to obtain:
 - $P = VI$
 $= V \times V/R$
 $= V^2 / R$

3-9: Power Formulas

- Applying Power Formulas:

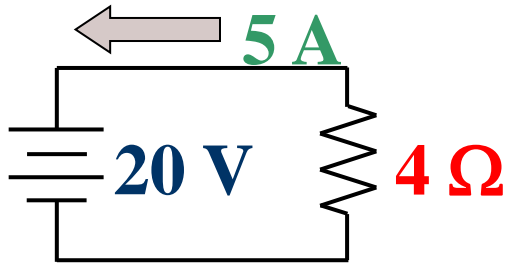

$$P = VI = 20 \times 5 = 100 \text{ W}$$

$$P = I^2 R = 25 \times 4 = 100 \text{ W}$$

$$P = \frac{V^2}{R} = \frac{400}{4} = 100 \text{ W}$$

3-10: Choosing a Resistor for a Circuit

- Follow these steps when choosing a resistor for a circuit:
 - Determine the required resistance value as $R = V / I$.
 - Calculate the power dissipated by the resistor using any of the power formulas.
 - Select a wattage rating for the resistor that will provide an adequate cushion between the actual power dissipation and the resistor's power rating.

3-10: Choosing a Resistor for a Circuit

- Maximum Working Voltage Rating
 - A resistor's maximum working voltage rating is the maximum voltage a resistor can withstand without internal arcing.
 - The higher the wattage rating of the resistor, the higher the maximum working voltage rating.

3-10: Choosing a Resistor for a Circuit

- Maximum Working Voltage Rating

- With very large resistance values, the maximum working voltage rating may be exceeded before the power rating is exceeded.
- For any resistor, the maximum voltage which produces the rated power dissipation is:


- $$V_{\max} = \sqrt{P_{\text{rating}} \times R}$$

3-11: Electric Shock


- When possible, work only on circuits that have the power shut off.
- If the power must be on, use only one hand when making voltage measurements.
- Keep yourself insulated from earth ground.
- Hand-to-hand shocks can be very dangerous because current is likely to flow through the heart!

3-12: Open-Circuit and Short-Circuit Troubles

An open circuit has zero current flow.

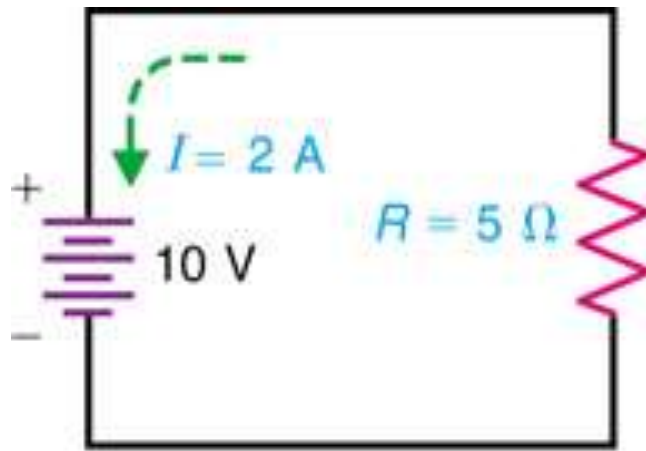

(a)

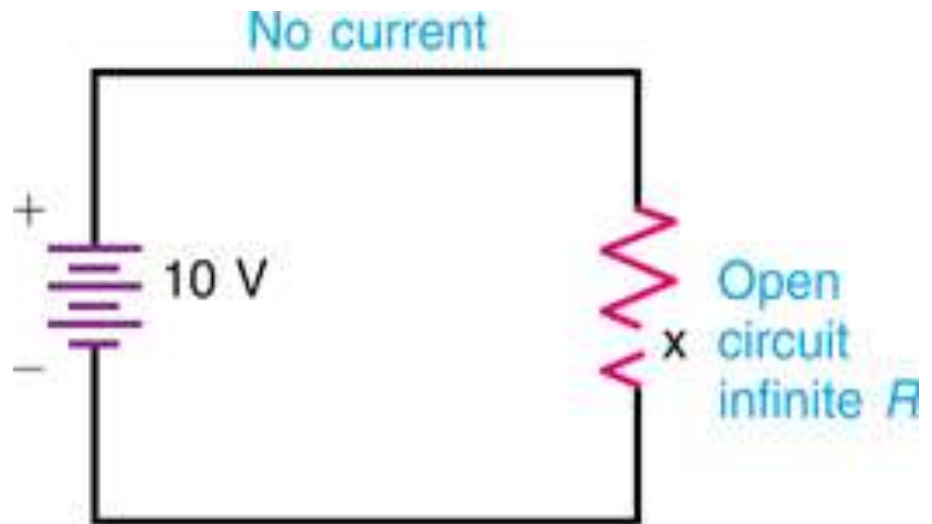

(b)

3-12: Open-Circuit and Short-Circuit Troubles

A short circuit has excessive current flow.

As R approaches 0, I approaches ∞ .

